

Question (01)

Q-01. The graph in Figure (Q-01) shows the charge $q(t)$ flowing past a point in a wire as a function of time

- (a) Sketch the variation of $i(t)$ versus time [Graph paper*]
- (b) Find the current $i(t)$ at 1; 2.5; 3.5; 4.5, and 5.5 msec


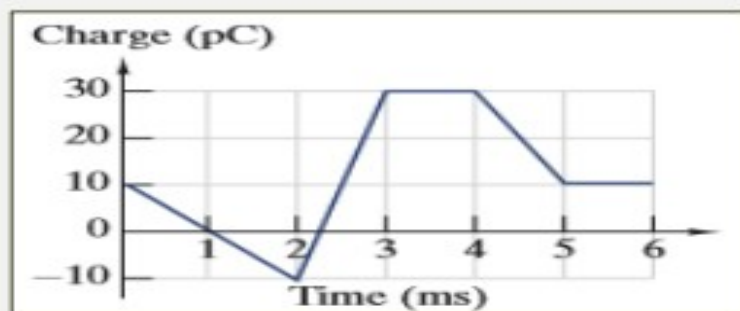


Figure Q-01

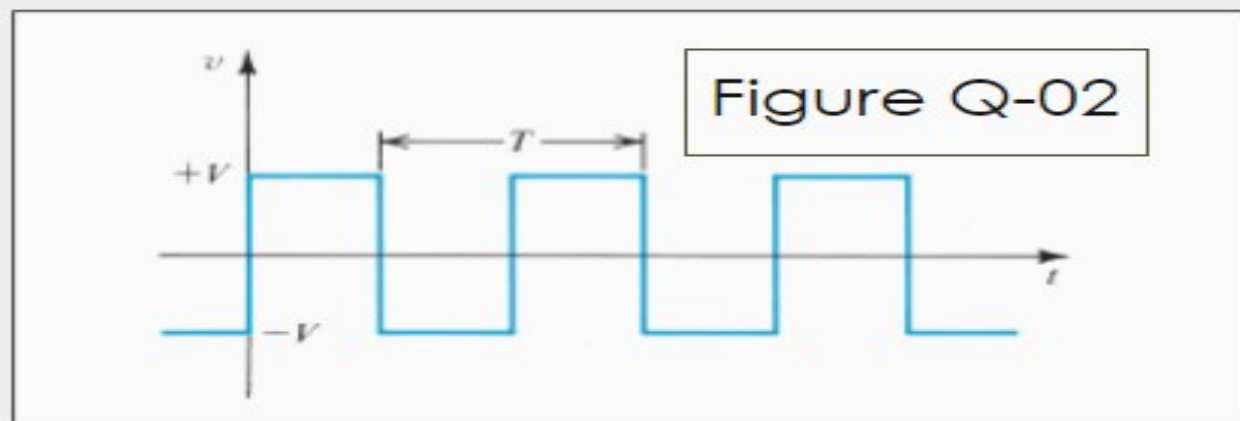Question (Q-02)

Q-02. (a) Identify the first five harmonics of the square wave $v(t)$ expressed in the Fig 1. Consider $V = +2$ Volt, $T = 628$ msec



- (b) What fraction of energy of $v(t)$ is in its fundamental?
- (c) What fraction of energy of $v(t)$ is in its first five harmonics?
- (d) In what number of harmonics is 90% of the energy?

Question (Q-03)

Q-03. (a) Find the time period and the cyclic and radian frequencies for each of the following sinusoids

$$v_1(t) = 17 \cos(2000t - 30^\circ)$$

$$v_2(t) = 12 \cos(2000t + 30^\circ)$$

(b) Derive the expression and sketch the graph of

$$v_3(t) = v_1(t) + v_2(t) \text{ [Graph Paper, Software Plot]}$$

Question (Q-04)

Q-04. Graphically sketch the waveform described


$$v(t) = \frac{r(t)}{T_c} \left[V_A e^{-\frac{t}{T_c}} \right] u(t) \text{ Volt}$$

[Graph Paper, Software Plot]

$$V_A = 1 \text{ Volt}, T_c = 1 \text{ sec}$$

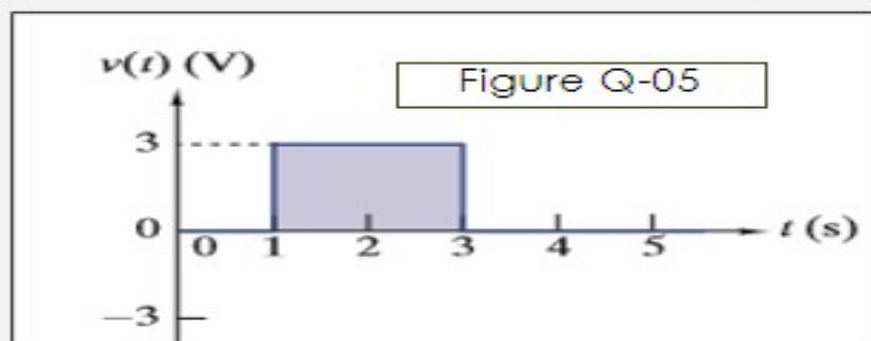Question (Q-05)

Q-05(a) Express the Gated Pulse Waveform of Fig.Q-05 in terms of Step functions $u(t)$.



(b) Determine the expression and graphically sketch the derivative of the gated pulse waveform shown in Fig.2
[Graph Paper, Software Plot]

(c) Determine the expression and graphically sketch the integral of the gated pulse waveform shown in Fig.2
[Graph Paper, Software Plot]

Question (Q-06)

Q-06. (a) Plot $v(t)$ expressed by

$$v(t) = 10[e^{-1000t} - e^{-2500t}]u(t)$$

[Graph Paper, Software Plot]

(b) What is the value of $v(t)$ at the extremum and the **time** when it occurs?

Question (Q-07)

Q-07. Find equivalent resistance seen from terminal A-B using Y - Δ transformation in Figure (Q-07); $R_L = 10\ \Omega$;
($R_{AB} = 27.18\ \Omega$)

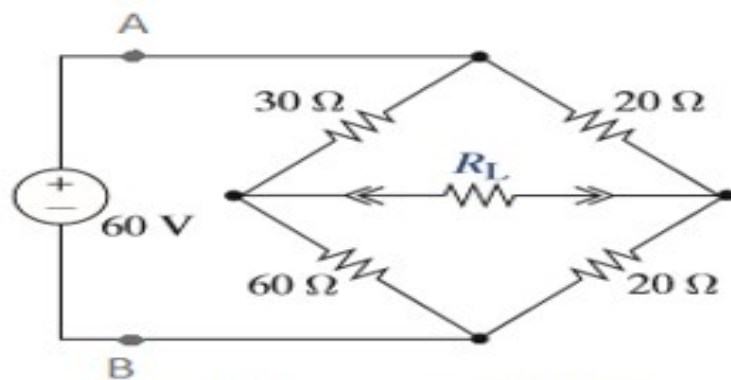


Figure Q-07

Question (Q-08)

Q-08. For a second-order low pass filter derived by cascading two first order RC low pass filter stage connected through an isolator or buffer stage with Gain, $A_v = 1$ as shown below. Assume that the capacitor is at a zero state initially i.e. $V_C(t = 0) = 0$ V.

(a) Draw s-domain transformed circuit for the filter.


(b) Find transfer function in s-domain for Stage (I), Stage (II) and overall transfer function i.e. $T_I(s) = \frac{V_X(s)}{V_I(s)}$, $T_{III}(s) = \frac{V_O(s)}{V_X(s)}$ and $T(s) = \frac{V_O(s)}{V_I(s)}$ respectively

(c) Hence find transfer function for physical frequencies i.e $T(j\omega)$ by $s = j\omega$ and derive expression for magnitude response, $|T(j\omega)|$

(d) Also calculate the corner frequency, ω_o for the filter.

(e) Find the transmission or gain at $\frac{\omega}{\omega_o} = 0.1$, $\frac{\omega}{\omega_o} = 1$ and at $\frac{\omega}{\omega_o} = 10$

(f) Plot magnitude response, $|T(j\omega)|$ vs. $\frac{\omega}{\omega_o}$.

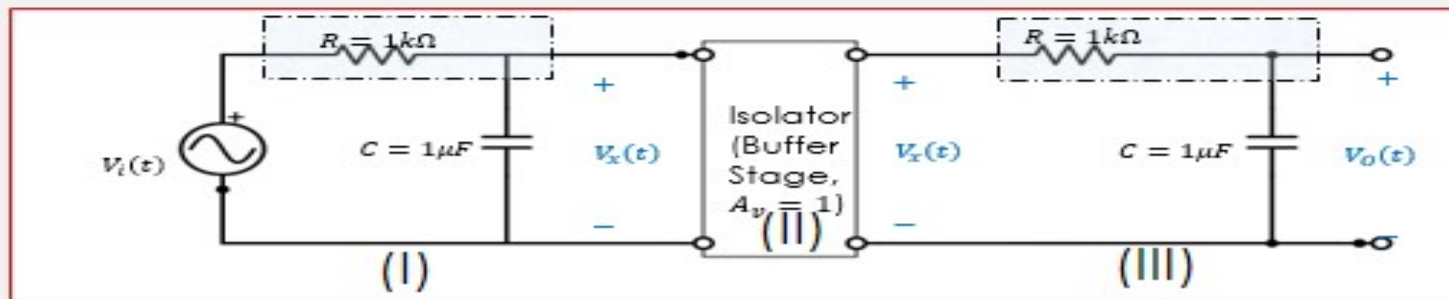

Question (Q-09)

Q-09. For the second-order series R - L - C resonator circuit as shown below,

(a) Draw s-domain transformed circuit for the resonator


(b) Find impedance offered by the circuit in s-domain i.e. $Z(s) = \frac{V_I(s)}{I_I(s)}$

(c) Hence find impedance for physical frequencies i.e. $Z(j\omega)$ by considering $s = j\omega$ and derive expression for magnitude response, $|Z(j\omega)|$

(d) Determine the resonant frequency, ω_o where the circuit offers purely resistive impedance

(e) Plot $|Z(j\omega)|$ and $|Y(j\omega)| = \frac{1}{|Z(j\omega)|}$ versus normalised frequency, $\frac{\omega}{\omega_o}$

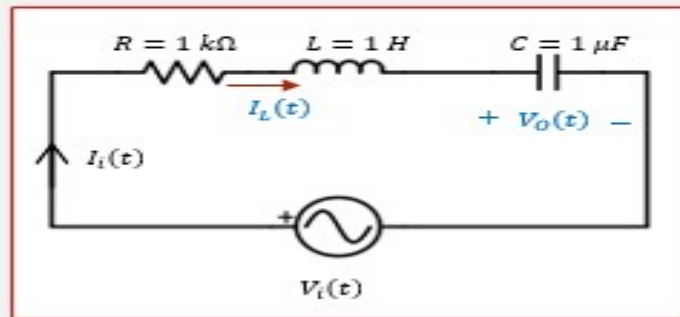Assume that the inductor and capacitor are at zero state initially i.e. $I_L(t = 0) = 0 \text{ A}$ and $V_C(t = 0) = 0 \text{ V}$



Question (Q-10)

Q-10. Figure Q-10 shows the voltage across a $0.5\mu\text{F}$ capacitor. Determine the time varying current, energy and power of the capacitor [GP/S]

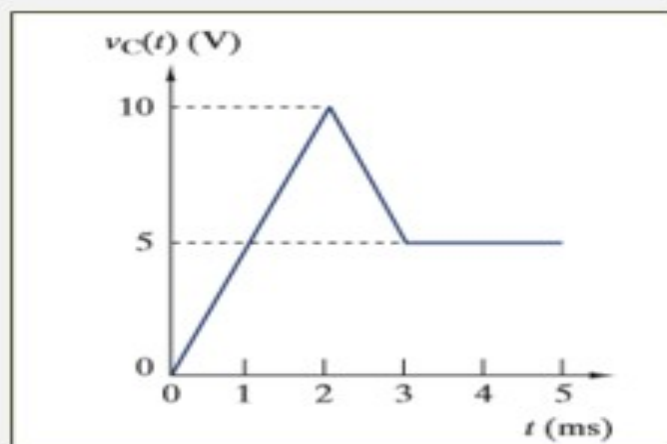


Fig. Q-10

Question (Q-11)

Q-11. The current through a 2.5-mH inductor

$$i(t) = 10 \cdot (e^{-500t}) \cdot (\sin 2000t)$$

Plot the waveforms of the element current, voltage, power, and energy. [GP/S]