

(b) No. of independent KCL equations = $N - 1 = 1$
No. of independent KVL equations = $E - N + 1 = 2$

(c) KCL Constraints:

$$\text{Node A: } I_{\text{in}} + I_y + I_o = 0 \Rightarrow I_y + I_o = -I_{\text{in}}$$

Element Constraints:

$$I_x = I_S = I_{\text{in}} \text{ , } I_y = \frac{V_A}{R} \text{ , } I_o = \frac{V_A}{2R} ; R = 1k\Omega$$

Nodal Equation

$$\text{Node A: } I_y + I_o = -I_{\text{in}}$$

$$\Rightarrow \frac{V_A}{R} + \frac{V_A}{2R} = -I_{\text{in}}$$

$$\Rightarrow \frac{3V_A}{2R} = -I_{\text{in}}$$

$$\Rightarrow V_A = -\frac{I_{\text{in}} \times 2 \times 1000}{3} = -\frac{2}{3} V$$

$$\bullet V_y = V_A = -\frac{2}{3} V$$

$$\bullet I_o = \frac{V_A}{2R} = \frac{-2}{3 \times 2 \times 1000} = -\frac{1}{3000} A$$

$$\bullet V_o = V_A = -\frac{2}{3} V$$


$$= -0.33 \text{ mA}$$

$$\bullet I_x = I_S = I_{\text{in}} =$$

$$\bullet I_y = \frac{V_A}{R} = -0.67 \text{ mA}$$

② Sol:-

$$R_s = 1000 \Omega$$

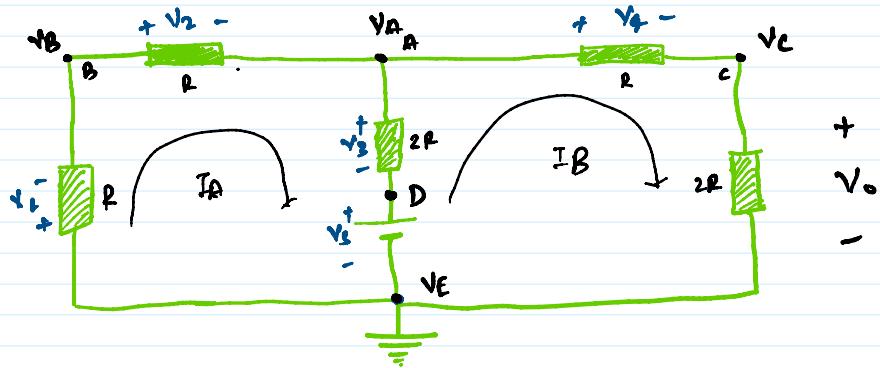

(a) No. of Nodes = 5 ; No. of Elements = 6

$$\text{No. of Loops} = E - N + 1 = 6 - 5 + 1 = 2.$$

(b) No. of independent KCL equations = $N - L = 4$

No. of independent KVL equations = $E - N + 1 = 2$

(c)

KVL Constraints

$$\text{Mesh A: } -V_1 - V_2 - V_3 - V_S = 0$$

$$\Rightarrow V_1 + V_2 + V_3 = -V_S$$

$$\text{Mesh B: } V_S + V_3 - V_4 - V_0 = 0$$

$$\Rightarrow V_3 - V_4 - V_0 = -V_S$$

Element Constraints

$$V_1 = I_A \cdot R; V_2 = I_A \cdot R; V_3 = (I_A - I_B) \cdot 2R; V_4 = I_B \cdot R$$

$$V_0 = I_B \cdot 2R$$

Mesh-Current Equations

$$\text{Mesh A: } V_1 + V_2 + V_3 = -V_S$$

$$\Rightarrow I_A \cdot R + I_A \cdot R + 2(I_A - I_B) \cdot R = -V_S$$

$$\Rightarrow 4I_A R - 2I_B R = -V_S$$

... (i)

$$M\Omega B: \quad \sqrt{3} - \sqrt{4} - V_0 = -\sqrt{3}$$

$$\rightarrow 2R(I_A - I_B) - I_B \cdot R - 2I_B R = -\sqrt{3}$$

$$\rightarrow 2I_A R - 5I_B R = -\sqrt{3}$$

- - (iii)

$$\begin{bmatrix} 4R & -2R \\ 2R & -5R \end{bmatrix} \begin{bmatrix} I_A \\ I_B \end{bmatrix} = \begin{bmatrix} -\sqrt{3} \\ -\sqrt{3} \end{bmatrix}$$

$$I_A = \frac{\begin{vmatrix} -\sqrt{3} & -2R \\ -\sqrt{3} & -5R \end{vmatrix}}{\begin{vmatrix} 4R & -2R \\ 2R & -5R \end{vmatrix}} = \frac{\begin{vmatrix} -4 & -2000 \\ -4 & -5000 \end{vmatrix}}{\begin{vmatrix} 4000 & -2000 \\ 2000 & -5000 \end{vmatrix}} = \frac{\frac{20000 - 8000}{-20000000 + 40000000}}$$

$$= \frac{12000}{-16000000} = -\frac{3}{4} \text{ mA}$$

$$I_B = \frac{\begin{vmatrix} 4R & -\sqrt{3} \\ 2R & -\sqrt{3} \end{vmatrix}}{\begin{vmatrix} 4R & -2R \\ 2R & -5R \end{vmatrix}} = \frac{\begin{vmatrix} 4000 & -4 \\ 2000 & -4 \end{vmatrix}}{-16000000} = \frac{-16000 + 8000}{-16000000}$$

$$= -\frac{1}{2} \text{ mA}$$

- $V_0 = I_B \times 2R = \frac{1}{2} \times 10^3 \times 2 \times 1000 = 1V$


- $I_o = I_B = 0.5 \text{ mA}$

③ Ans: ④



③ ~~Ans~~

a)

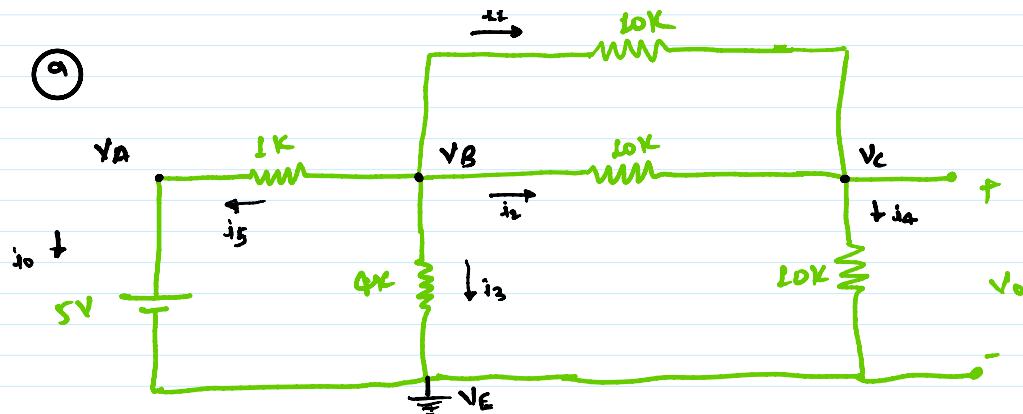

$$\text{No. of Nodes} = 4$$

$$\text{No. of KVL equations} = N-L = 4-1 = 3$$

KCL Constraints

$$\text{Node A: } i_0 - i_5 = 0$$

$$\text{Node B: } i_1 + i_2 + i_3 + i_5 = 0$$

$$\text{Node C: } i_4 - i_2 - i_3 = 0$$

Element Constraints

$$i_5 = \frac{V_B - V_A}{R}; \quad i_1 = \frac{V_B - V_C}{20R}; \quad i_2 = \frac{V_B - V_C}{10R}; \quad i_3 = \frac{V_B}{4R}; \quad i_4 = \frac{V_C}{20R}$$

$$\text{where } R = 1k\Omega; \quad V_A = 5V$$

Node-Voltage Equations

$$\text{Node B: } i_1 + i_2 + i_3 + i_5 = 0$$

$$\Rightarrow \frac{V_B - V_C}{20R} + \frac{V_B - V_C}{10R} + \frac{V_B}{4R} + \frac{V_B - V_A}{R} = 0$$

$$\Rightarrow 2V_B - 2V_C + 2V_B - 2V_L + 5V_B + 20V_B - 20V_A = 0$$

$$\Rightarrow -20V_A + 29V_B - 4V_C = 0$$

$$\Rightarrow -20 \times 5 + 29V_B - 4V_C = 0$$

$$\Rightarrow \underline{29V_B - 4V_C = 100} \quad - \text{(i)}$$

$$\text{Node C: } i_4 - i_2 - i_3 = 0$$

$$\Rightarrow \frac{V_C}{20R} - \frac{V_B - V_C}{10R} - \frac{V_B - V_C}{20R} = 0$$

$$\Rightarrow V_C - V_B + V_C - V_B + V_C = 0$$

$$\Rightarrow -2VB + 3VC = 0 \quad - (ii)$$

from (i) and (ii)

$$29VB - 9VC = 100$$


$$\Rightarrow 29 \cdot \frac{3VC}{2} - 9VC = 100$$

$$\Rightarrow \frac{79VC}{2} = 100 \Rightarrow VC = \frac{200}{79} V$$

$$\text{So, } VB = \frac{3VC}{2} = \frac{3}{2} \times \frac{200}{79} = \frac{300}{79} V.$$

$$\bullet \quad VO = VC = \frac{200}{79} V = 2.53V$$

(b)

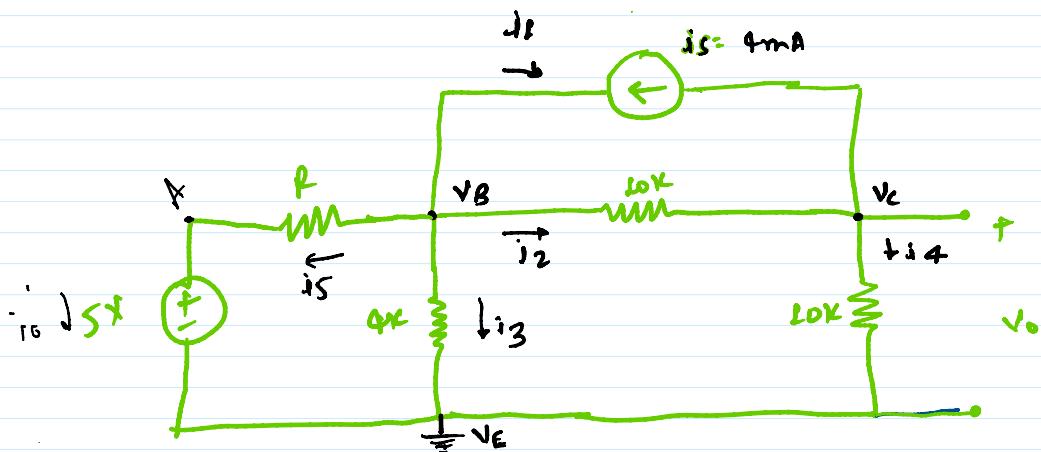

KCL Constraints

$$\text{Node A: } i_0 - i_5 = 0$$

$$\text{Node B: } i_1 + i_2 + i_3 + i_5 = 0$$

$$\text{Node C: } i_4 - i_2 - i_3 = 0$$

Element Constraints

$$i_5 = \frac{VB - VA}{R}; \quad i_2 = -i_5; \quad i_1 = \frac{VB - VC}{20k}; \quad i_3 = \frac{VB}{4k}; \quad i_4 = \frac{VC}{20k}$$

$$\text{where } R = 1k\Omega; \quad VA = 5V$$

Node-Voltage Equations

$$\text{Node B: } i_1 + i_2 + i_3 + i_5 = 0$$

$$\Rightarrow \underline{VB - VC} + \underline{VB} + \underline{VB - VA} = i_5$$

$$\Rightarrow \frac{V_B - V_C}{10R} + \frac{V_B}{4R} + \frac{V_B - V_A}{R} = i_s$$

$$\Rightarrow 2V_B - 2V_C + 5V_B + 20V_B - 20V_A = i_s \cdot 20R$$

$$\Rightarrow -20V_A + 27V_B - 2V_C = 20i_s R$$

$$\Rightarrow -20 \cdot 5 + 27V_B - 2V_C = 4 \times 10^{-3} \times 20 \times 1000$$

$$\Rightarrow 27V_B - 2V_C = 180 \quad - (ii)$$

Node C:

$$j_4 - j_2 - j_1 = 0$$

$$\Rightarrow \frac{V_C}{10R} - \frac{V_B - V_C}{10R} = -i_s$$

$$\Rightarrow -V_B + 2V_C = -i_s \cdot 20R$$

$$\Rightarrow -V_B + 2V_C = -4 \times 10^{-3} \times 20 \times 1000 = -80$$

$$\Rightarrow -V_B + 2V_C = -80 \quad - (iii)$$

adding (i) and (ii)


$$26V_B = 180$$

$$V_B = \frac{180}{26} = 5.38 \text{ V}$$

$$V_C = \frac{V_B - 80}{2} = -17.30 \text{ V}$$

$$\bullet V_A = V_C = -17.30 \text{ V}$$

(4) (i) (a)

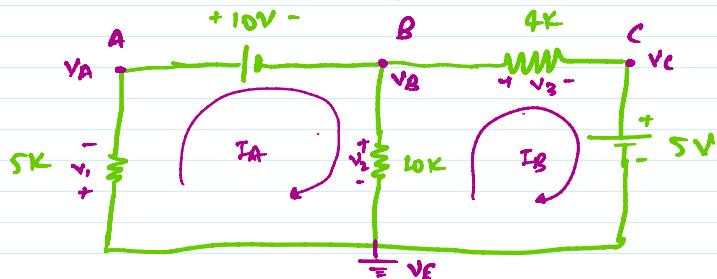

No. of elements = 5

No. of nodes = 4

No. of MC Eq's = $5 - 1 + 1 = 2$

KVL Constraints

$$\text{Mesh A: } -V_L - V_{S_1} - V_2 = 0$$

$$\Rightarrow -V_L - V_2 = V_{S_1}$$

$$\text{Mesh B: } V_2 - V_3 - V_{S_2} = 0 \Rightarrow V_2 - V_3 = V_{S_2}$$

Element Constraints

$$V_{S_1} = 10V; V_{S_2} = 5V; V_L = 5R \cdot I_A; V_2 = 20R(I_A - I_B); V_3 = 4R \cdot I_B$$

Mesh Current Equations

$$\text{Mesh A: } -V_1 - V_2 = V_{S_1}$$

$$\Rightarrow -5R I_A - 20R(I_A - I_B) = 10$$

$$\Rightarrow -5R I_A - 10R I_A + 10R I_B = 10$$

$$\Rightarrow -15R I_A + 10R I_B = 10$$

$$\Rightarrow -3R I_A + 2R I_B = 2 \quad \dots \text{(i)}$$

$$\text{Mesh B: } V_2 - V_3 = V_{S_2}$$

$$\Rightarrow 20R(I_A - I_B) - 4R I_B = 5$$

$$\Rightarrow 20R \cdot I_A - 14R \cdot I_B = 5 \quad \dots \text{(ii)}$$


$$\begin{bmatrix} -3R & 2R \\ 20R & -14R \end{bmatrix} \begin{bmatrix} I_A \\ I_B \end{bmatrix} = \begin{bmatrix} 2 \\ 5 \end{bmatrix}$$

$$I_A = \frac{\begin{vmatrix} 2 & 2R \\ 5 & -14R \end{vmatrix}}{\begin{vmatrix} -3R & 2R \\ 20R & -14R \end{vmatrix}} = \frac{\begin{vmatrix} 2 & 2000 \\ 5 & -14000 \end{vmatrix}}{\begin{vmatrix} -3000 & 2000 \\ 20000 & -14000 \end{vmatrix}} = \frac{-28000 - 10000}{(42 - 20) \times 10^6}$$

$$= \frac{-38000}{22 \times 10^6} = -1.72 \text{ mA}$$

$$I_B = \frac{\begin{vmatrix} -3R & 2 \\ 10R & 5 \end{vmatrix}}{\begin{vmatrix} -3R & 2R \\ 10R & -10R \end{vmatrix}} = \frac{\begin{vmatrix} -3000 & 2 \\ 10000 & 5 \end{vmatrix}}{\begin{vmatrix} 22 \times 10^6 & \\ \end{vmatrix}} = \frac{-15000 - 20000}{22 \times 10^6} = -1.59 \text{ mA}$$

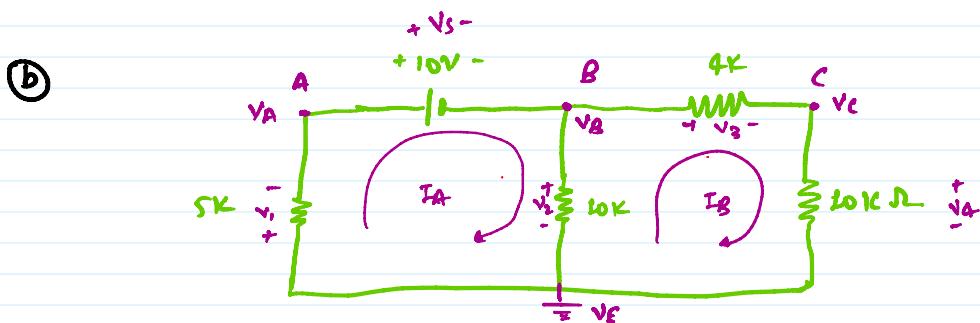• $I_o = I_A - I_B = -1.72 - (-1.59) = -0.13 \text{ mA}$



No. of elements = 5

No. of nodes = 4

No. of MC Eqns = $5 - 4 + 1 = 2$

KVL Constraints

MESH A: $-V_L - V_S - V_2 = 0$

$$\Rightarrow -V_L - V_2 = V_S$$

MESH B: $V_2 - V_3 - V_4 = 0$

Element Constraints

$$V_S = 10V ; V_L = 5R \cdot I_A ; V_2 = 10R(I_A - I_B) ; V_3 = 4R \cdot I_B ; V_4 = I_B \cdot 20k$$

MESH - Current Equations

MESH A: $-V_L - V_2 = V_S$

$$\Rightarrow -5R I_A - 10R I_A + 10R I_B = V_S$$

$$\Rightarrow -15R \cdot I_A + 10R \cdot I_B = 10$$

$$\Rightarrow -3R I_A + 2R I_B = 2 \quad \text{--- (i)}$$

MESH B: $V_2 - V_3 - V_4 = 0$

$$\Rightarrow 20R(I_A - I_B) - 4R I_B - I_B \cdot 20R = 0$$

$$\Rightarrow 20R \cdot I_A - 24R I_B = 0 \quad - \text{(I)}$$


$$\begin{bmatrix} -3R & 2R \\ 20R & -24R \end{bmatrix} \begin{bmatrix} I_A \\ I_B \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \end{bmatrix}$$

$$I_A = \frac{\begin{vmatrix} 2 & 2R \\ 0 & -24R \end{vmatrix}}{\begin{vmatrix} -3R & 2R \\ 20R & -24R \end{vmatrix}} = \frac{-48R}{72R^2 - 20R^2} = \frac{-48}{52} = -\frac{48}{52} \text{ mA} = -\frac{9}{52} \text{ mA}$$



$$I_B = \frac{\begin{vmatrix} -3R & 2 \\ 20R & 0 \end{vmatrix}}{\begin{vmatrix} -3R & 2R \\ 20R & -24R \end{vmatrix}} = \frac{-20R}{52R^2} = \frac{-20}{52} \text{ mA}$$

$$\bullet \quad I_0 = I_A - I_B = -\frac{98 + 20}{52} \text{ mA} = \frac{-28}{52} \text{ mA} = -0.538 \text{ mA}$$

(5) (a)

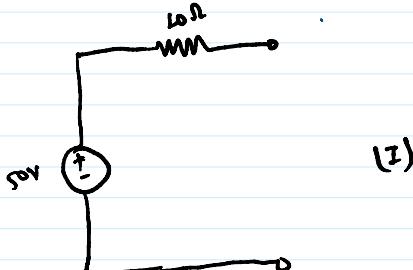


(II)


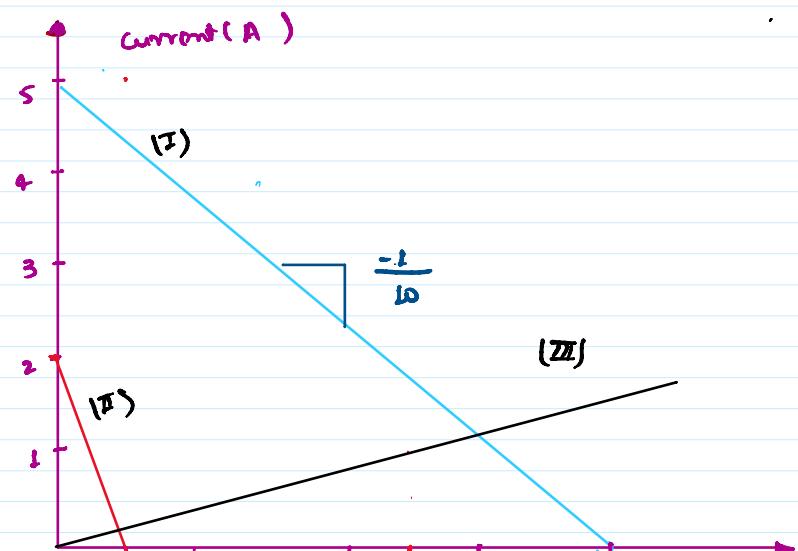
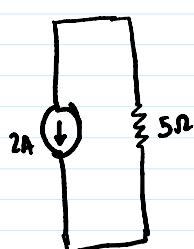




!

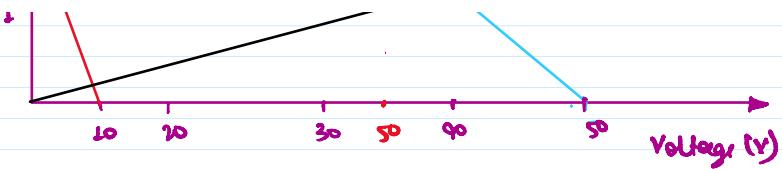


b

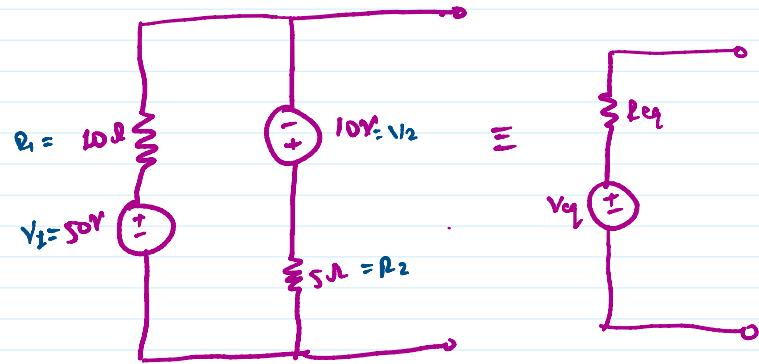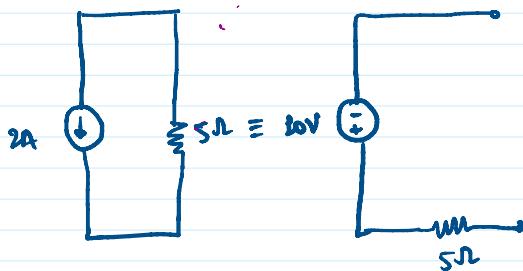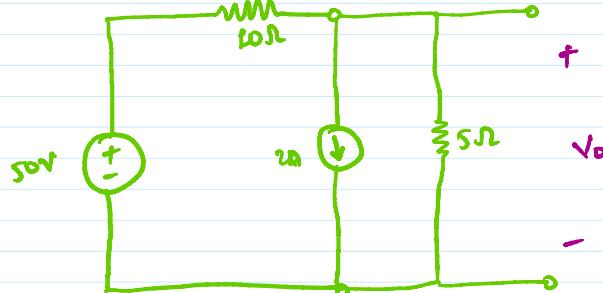


$$\begin{aligned}
 V_{eq} &= \frac{V_1 R_2 + V_2 R_1}{R_1 + R_2} \\
 &= \frac{50 \cdot 5 + (-10) \cdot 10}{10 + 5} \\
 &= \frac{250 - 100}{15} = \frac{150}{15} = 10V
 \end{aligned}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = \frac{5 \times 10}{15} = \frac{10}{3} \Omega$$

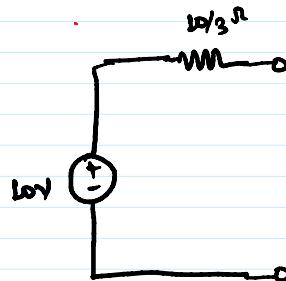• Equivalent practical voltage source circuit :-




c

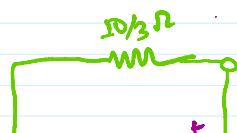

$$V_o = \frac{5}{5+10} \times 10$$

(c)

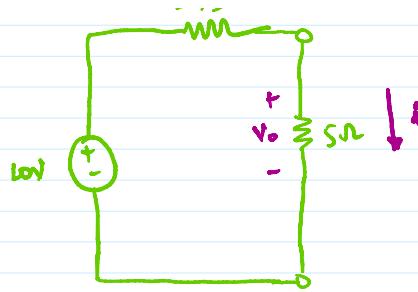


$$V_o = \frac{5}{5 + \frac{10}{3}} \times 10 = \frac{15^3}{25} \times 10^2 = 6V$$

$$I = \frac{V_o}{R_1} = \frac{6}{5} = 1.2A$$

$$\text{power} = V_o I_o = (6 \times 1.2) W = 7.2W$$

(6)

(a)

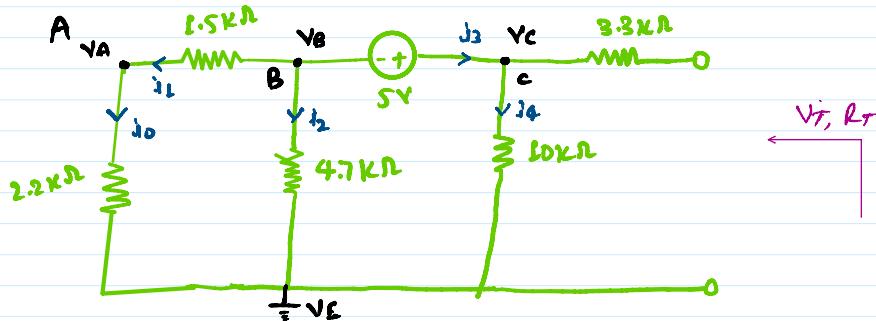

No. of nodes = 4

No. of KVL eqns = 3

KCL Constraint

$$\text{Node A: } j_0 - j_1 = 0$$

$$\text{Node B: } j_1 + j_2 + j_3 = 0$$

$$\text{Node C: } j_4 - j_3 = 0 \Rightarrow j_3 = j_4$$

Element Constraints

$$j_0 = \frac{V_A}{2200} ; j_1 = \frac{V_B - V_A}{1500} ; j_4 = \frac{V_C}{10000} ; V_C - V_B = 5V ; j_2 = \frac{V_B}{4700}$$

Node-Voltage equations:

$$\text{Node A: } j_0 - j_1 = 0$$

$$\Rightarrow \frac{V_A}{2200} - \frac{V_B - V_A}{1500} = 0$$

$$\Rightarrow 15V_A = 22V_B - 22V_A$$

$$\Rightarrow 37V_A - 22V_B = 0$$

$$\text{Node B: } j_1 + j_2 + j_3 = 0$$

$$\frac{V_B - V_A}{1500} + \frac{V_B}{4700} + \frac{V_C}{10000} = 0$$

$$\frac{V_B - V_A}{15} + \frac{V_B}{47} + \frac{V_C}{100} = 0$$

$$4700V_B - 4700V_A + 1500V_B + 705V_C = 0$$

$$\Rightarrow -940V_A + 1240V_B + 141V_C = 0$$

and

$$-V_B + V_C = 5$$


$$\begin{bmatrix} .37 & -22 & 0 \\ 0 & -1 & 1 \\ -940 & 1240 & 101 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} 0 \\ 5 \\ 0 \end{bmatrix}$$

$$V_A = \frac{\begin{vmatrix} 0 & -22 & 0 \\ 5 & -1 & 1 \\ 0 & 1240 & 101 \end{vmatrix}}{\begin{vmatrix} 37 & -22 & 0 \\ 0 & -1 & 1 \\ -940 & 1240 & 101 \end{vmatrix}} = \frac{77550}{-152085} = -0.509 \text{ V}$$

$$V_B = \frac{\begin{vmatrix} 37 & 0 & 0 \\ 0 & 5 & 1 \\ -940 & 0 & 101 \end{vmatrix}}{\begin{vmatrix} 37 & -22 & 0 \\ 0 & -1 & 1 \\ -940 & 1240 & 101 \end{vmatrix}} = \frac{230425}{-152085} = -0.8575 \text{ V}$$

$$V_C = V_B + 5 = -0.8575 + 5 = 4.142 \text{ V}$$

$$V_T = V_C = 4.142 \text{ V}$$

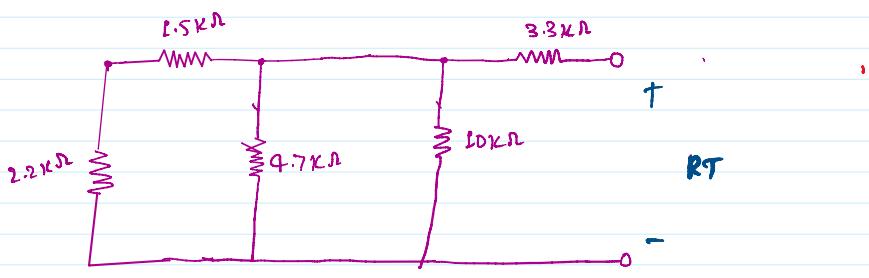

$$RT = ((1.5\text{k} + 2.2\text{k}) \parallel 4.7\text{k}) \parallel 10\text{k} + 3.3\text{k}$$


$$= (3700 \parallel 4700 \parallel 10000) + 3.3\text{k}$$

$$= \left[\left(\frac{3700 \cdot 4700}{3700 + 4700} \right) \parallel 10000 \right] + 3300$$

$$= (2070.23 / 10000) + 3300$$

$$= 1715.15 + 3300 \approx \underline{\underline{5015 \Omega}}$$

(b)

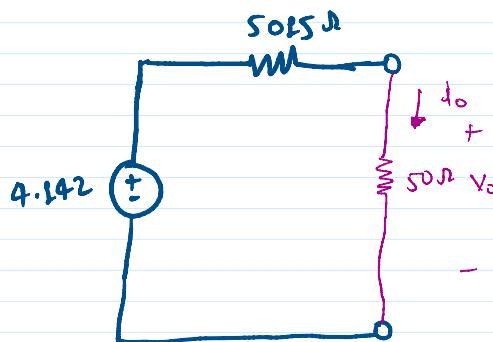

$$I_o = \frac{4.142}{5015 + 50} = 0.817 \text{ mA}$$

$$V_o = I_o \cdot R = 50 \cdot I_o$$

$$= 50 \times 0.817 \text{ mV}$$


$$= 40.8 \text{ mV}$$

$$\text{Power} = V_o I_o = 40.8 \times 0.817 \text{ mW}$$

$$= 33.33 \text{ mW}$$

$$I_o = 0.817 \text{ mA} ; V_o = 40.8 \text{ mV} ; \text{Power} = 33.33 \text{ mW}$$

(7) (a)

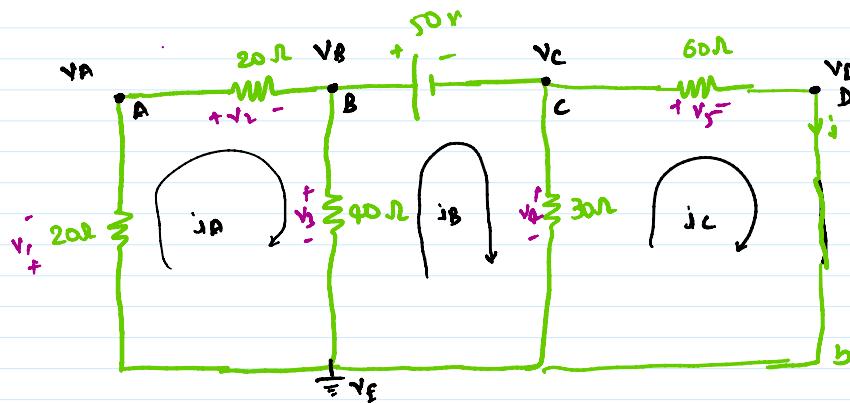

Total No. of elements, E = 6

Total No. of nodes, N = 5

Total No. of independent mesh equation = 6 - 5 + 1 = 2.

(b)

KVL constraints

$$\text{Mesh A: } -V_1 - V_2 - V_3 = 0 \Rightarrow V_1 + V_2 + V_3 = 0$$

$$\text{Mesh B: } V_3 - V_4 - V_5 = 0 \Rightarrow V_3 - V_4 = V_5$$

$$\text{Mesh C: } V_4 - V_5 = 0$$

Element constraints

$$V_1 = 20jA; V_2 = 20jA; V_3 = (jA-jB) \cdot 90; V_4 = (jB-jC) \cdot 30; V_5 = jC \cdot 60$$

Mesh Current Equation

$$\text{Mesh A: } V_1 + V_2 + V_3 = 0$$

$$\Rightarrow 20jA + 20jA + 90jA - 90jB = 0$$

$$\Rightarrow 80jA - 90jB = 0$$

$$\Rightarrow 8jA - 9jB = 0$$

- (i)

$$\text{Mesh B: } V_3 - V_4 = V_5$$

$$\Rightarrow 40(jA - jB) - 30(jB - jC) = 50$$

$$\Rightarrow 40jA - 70jB + 30jC = 50$$

$$\Rightarrow 4jA - 7jB + 3jC = 5 \quad - (ii)$$

$$\text{Mesh C: } V_4 - V_5 = 0 \Rightarrow (jB - jC) \cdot 30 - 60jC = 0$$

$$\Rightarrow 30jB - 90jC = 0$$

$$\Rightarrow jB - 3jC = 0 \quad - (iii)$$

adding (i) and (iii)

$$2jA - 3jC = 0 \quad - (iv)$$

from (ii) and (iv)

$$4jA - 7(3jC) + 3jC = 5$$

$$\Rightarrow 4jA - 18jC = 5$$

- (v)


Two independent eqn are (iv) and (v)

from (iv) and (v)

$$\left. \begin{array}{l} 4jA - 18jC = 5 \\ \Rightarrow 2 \cdot (3jC) - 18jL = 5 \\ \Rightarrow -12jL = 5 \end{array} \right\} \Rightarrow jL = \frac{-5}{12} \text{ A}$$

$$jN = jC = -5/12 \text{ A}$$

(c)

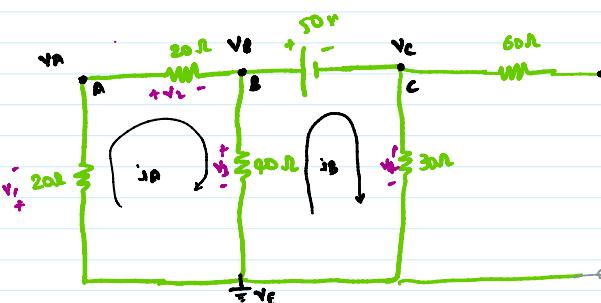

Total No. of Elements = 5

Total No. of Nodes = 4

Total No. of independent

Mesh Current equation = 5 - 4 + 1
= 2

KVL Constraints

$$\text{Mesh A: } -v_1 - v_2 - v_3 = 0 \Rightarrow v_1 + v_2 + v_3 = 0$$

$$v_1 = 20jA; v_2 = 20jA; v_3 = 40(jA - jB)$$

$$\text{Mesh B: } v_3 - v_4 - v_1 = 0 \Rightarrow v_3 - v_4 = v_1$$

$$v_4 = 30jB$$

Element Constraints

$$\text{Mesh A: } v_1 + v_2 + v_3 = 0$$

$$\text{Mesh B: } v_3 - v_4 = v_1$$

$$\Rightarrow 20jA + 20jA + 40jA - 40jB = 0$$

$$\Rightarrow 40jA - 40jB - 30jB = 50$$

$$\Rightarrow 80jA - 90jB = 0$$

$$\Rightarrow 40jA - 70jB = 50$$

$$\Rightarrow 2jA - jB = 0 \quad \text{(i)}$$

$$\Rightarrow 4jA - 7jB = 5 \quad \text{(ii)}$$

Putting (i) in (ii)

$$2jB - 7jB = 5$$


$$jB = -1A$$

$$v_T = v_C = 30 \cdot 1B = -30V$$


(d)
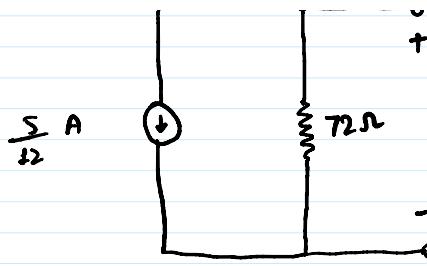
$$R_T = \frac{v_T}{i_m} = \frac{-30}{-5/12} = 6 \times 12 = 72\Omega$$





(e)

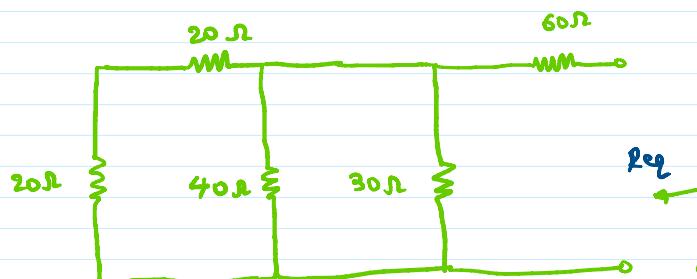

Look-back method

$$R_{eq} = \left[(20+20) \parallel 40 \parallel 30 \right] + 60$$

$$= \left[40 \parallel 40 \parallel 30 \right] + 60$$


$$= \left[\frac{1600}{80} \parallel 30 \right] + 60$$

$$= (20 \parallel 30) + 60$$

$$= \cancel{\frac{20 \cdot 30}{50}} + 60 = 72 \Omega$$

$$R_{eq} = R_T = 72 \Omega$$

(d)

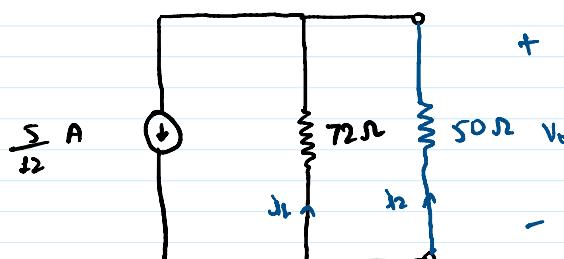

$$j_2 = \frac{72}{72+50} \times \frac{5}{50}$$

$$j_2 = \frac{30}{72+50} = \frac{30}{122} \text{ A}$$

$$j_2 = \frac{30}{122} \text{ A}$$


$$V_o = -j_2 \cdot 50 = -\frac{30}{122} \cdot 50 = -12.29 \text{ V}$$

$$V_2 = -12.29 \text{ V}$$


$$\text{Power} = |V_o \cdot I_R| = 3.023 \text{ mWatt}$$

$$P = 3.023 \text{ W}$$

(8)

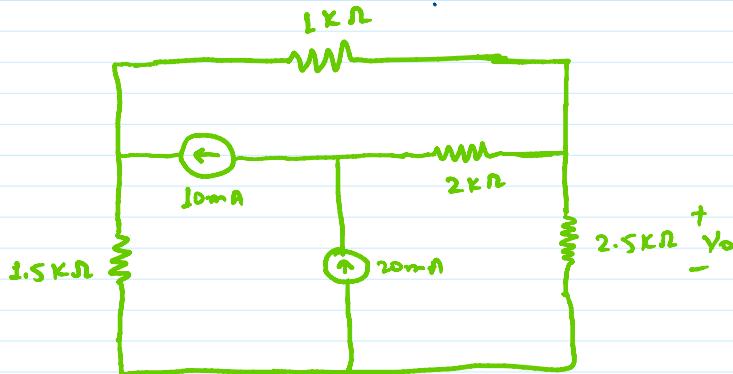

Super mesh

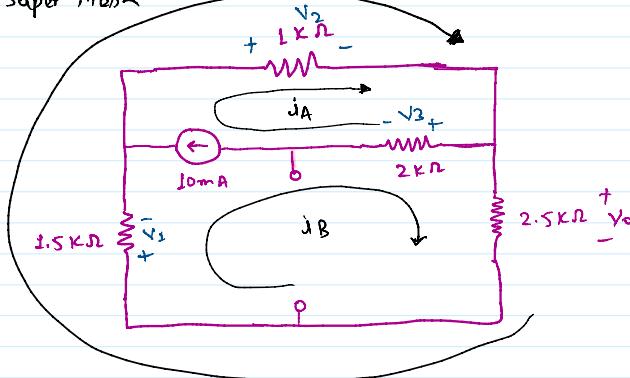

(I)

KVL Constraints

$$\text{Super mesh : } -V_1 - V_2 - V_{o1} = 0$$

$$V_1 + V_2 + V_{o1} = 0$$

Element Constraints

$$j_A - j_B = 10 \text{ mA} ; \quad V_1 = 1500 j_B$$

$$V_2 = 2000 j_A ; \quad V_{o1} = 2500 j_B$$

Mesh Current Equation


$$V_1 + V_2 + V_{o1} = 0$$

$$\Rightarrow 1500 j_B + 1000 j_A + 2500 j_B = 0$$

$$\Rightarrow 1000 j_A + 4000 j_B = 0$$

$$\Rightarrow j_A + 4 j_B = 0 \quad \text{--- (i)}$$

Super mesh

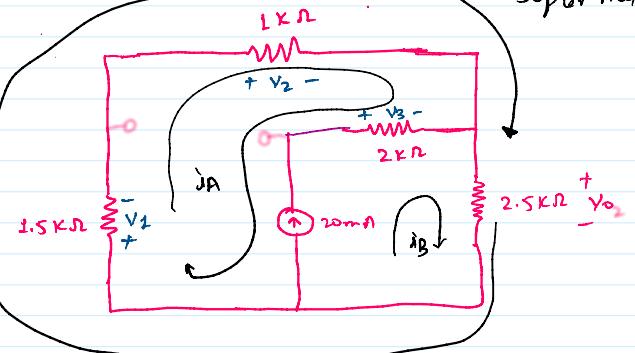

(II)

KCL Constraints

$$\text{Super mesh : } -V_1 - V_2 - V_{o2} = 0$$

$$V_1 + V_2 + V_{o2} = 0$$

Element Constraints

$$j_B - j_A = 20 \text{ mA} ; \quad V_1 = 1500 j_A ;$$

$$V_2 = 2000 j_A ; \quad V_{o2} = 2500 j_B$$

Mesh Current Equation

$$V_1 + V_2 + V_{o2} = 0$$

$$\Rightarrow 1500 j_A + 1000 j_A + 2500 j_B = 0$$

$$\Rightarrow j_A + 5 j_B = 0 \quad \text{--- (ii)}$$

$$\text{also, } j_B - j_A = 20 \text{ mA} \quad \text{--- (iii)}$$

$$\text{also, } i_A - i_B = 10\text{mA} \quad (\text{ii})$$

from (i) and (ii)

from (i) and (iii)

$$i_A = -10\text{mA}; i_B = 10\text{mA}$$

$$i_B = -2\text{mA}; i_A = 8\text{mA}$$

$$V_{O1} = 2500 i_B$$

$$= 2500 \times -2\text{mA}$$

$$= 10 \times 2.5 = 25\text{V}$$

$$V_{O1} = -5\text{V}$$

$$V_{O2} = 25\text{V}$$

- By superposition principle, we can say.

$$\text{Voltage across } 2.5\text{k}\Omega \text{ resistor, } V_0 = V_{O1} + V_{O2}$$

$$= 20\text{V}$$